

**DIPLOMA IN MECHANICAL ENGINEERING  
(DME)**

**Term-End Examination**

00638

**June, 2016**

**BEE-031 : ELECTRICAL TECHNOLOGY**

*Time : 2 hours*

*Maximum Marks : 70*

**Note :** *Question no. 1 is compulsory. Attempt any four of the remaining questions. Use of scientific calculator is allowed.*

1. (A) Choose the correct answer of the following :

7×1=7

- (a) At resonance frequency the impedance of R-L-C series circuit is
- (i)  $Z = X_L$
  - (ii)  $Z = X_C$
  - (iii)  $Z = R$
  - (iv)  $Z = 0$
- (b) A reciprocal network consists of
- (i) unilateral elements only
  - (ii) bilateral elements only
  - (iii) any type of network
  - (iv) None of the above


- (c) Resistance of armature winding in a DC machine is approximately in the range of
- (i) one ohm
  - (ii) 50 ohms
  - (iii) 1 k $\Omega$
  - (iv) 100 ohms
- (d) No-load current of a transformer is \_\_\_\_\_ % of the rated current.
- (i) 5
  - (ii) 10
  - (iii) 20
  - (iv) 50
- (e) A 3-phase induction motor normally operates equal to
- (i) 4% slip
  - (ii) 10% slip
  - (iii) 50% slip
  - (iv) 100% slip
- (f) In a 3-phase synchronous generator, voltage regulation is negative when the connected load is
- (i) pure resistive
  - (ii) inductive
  - (iii) capacitive
  - (iv) no load

- (g) Speed of rotor of a synchronous motor is
- (i) same as synchronous speed
  - (ii) less than synchronous speed
  - (iii) above synchronous speed
  - (iv) None of the above

(B) State *true* or *false* for the following statements : 7×1=7

- (a) Ideal independent voltage source has zero internal resistance.
- (b) Using principle of superposition, power calculation is possible in DC networks.
- (c) DC series motor never operates at no-load.
- (d) Core of a transformer is made of copper.
- (e) Speed of rotor in an induction motor is synchronous speed.
- (f) Synchronization of alternators is done by three dark lamps method.
- (g) Over-excited synchronous motor operates as leading power factor load.

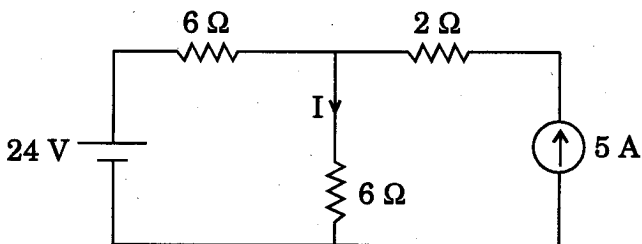2. (a) State and explain Thevenin's theorem. 7
- (b) Find the current  $I$  using superposition theorem. 7



3. (a) Discuss various methods used for speed control of a DC series motor. 7
- (b) A 6-pole wave-wound DC generator has 2 parallel paths in armature, each path contains 1000 conductors. If the armature rotates at 500 rpm and flux per pole is 0.05 Wb, calculate the emf induced in the armature. 7
4. (a) Draw the equivalent circuit of a transformer. Also draw the simplified equivalent circuit by referred total resistance and reactance of two windings in any one winding. 7
- (b) A 100 kVA transformer has 2 kW iron loss and 10 kW full load copper loss. Calculate the load at which the efficiency of the transformer is maximum. Also calculate the maximum efficiency. 7
5. (a) Draw a circuit diagram of a star delta starter used to start a 3-phase induction motor and explain its working. 7
- (b) A 3-phase induction motor has the following data :
- Power input to the stator = 20 kW  
Stator losses = 1 kW  
Mechanical losses = 1.5 kW  
Slip = 5%
- Calculate the output of the motor and its efficiency. 7

6. (a) Write the need of parallel operation of alternators. Explain any one method used for synchronization of two alternators. 7
- (b) Explain the requirement and working of a synchronous condenser. 7
7. Write short notes on any *two* of the following :  $2 \times 7 = 14$
- (a) 3-point starter of DC motor
- (b) Auto-transformer and its applications
- (c) Starting of synchronous motor
- (d) Merits of three-phase system
-