

**DIPLOMA – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI) /
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination

00786

June, 2016

BIEL-028 : CIRCUITS AND NETWORKS

Time : 2 hours

Maximum Marks : 70

Note : Attempt any five questions. Question no. 1 is compulsory. All questions carry equal marks. Symbols used have their usual meaning. Use of scientific calculator is permitted.

1. (a) Superposition theorem is valid only for
- (i) linear circuits
 - (ii) non-linear circuits
 - (iii) both linear and non-linear circuits
 - (iv) Neither of the two

- (b) Maximum power transfer occurs at
- (i) 100% efficiency
 - (ii) 50% efficiency
 - (iii) 25% efficiency
 - (iv) 75% efficiency
- (c) What is the phase angle of a series RLC circuit at resonance ?
- (i) Zero
 - (ii) 90°
 - (iii) 45°
 - (iv) 30°
- (d) The differential equation of an electric current in a circuit containing resistance R and a capacitor C in series with the voltage source V is given by

(i)
$$\frac{dV}{dt} = Ri + \int \frac{1}{C} idt$$

(ii)
$$\frac{dV}{dt} = R \frac{di}{dt} + \int \frac{1}{C} idt$$

(iii)
$$\frac{dV}{dt} = R \frac{di}{dt} + \frac{i}{C}$$

(iv)
$$V = R \frac{di}{dt} + \frac{i}{C}$$

- (e) The time constant of a series RL circuit is
- (i) LR
 - (ii) $\frac{L}{R}$
 - (iii) $\frac{R}{L}$
 - (iv) $e^{-R/L}$
- (f) The transfer impedance is defined as
- (i) the ratio of transform voltage to transform current at the same port
 - (ii) the ratio of transform voltage at one port to the transform current at the other port
 - (iii) Both (i) and (ii)
 - (iv) None of the above
- (g) For a two-port bilateral network, the three transmission parameters are given by $A = \frac{6}{5}$, $B = \frac{17}{5}$, and $C = \frac{1}{5}$. What is the value of D ?
- (i) 1
 - (ii) $\frac{1}{5}$
 - (iii) $\frac{7}{5}$
 - (iv) $\frac{11}{5}$

7×2=14

2. (a) Find the current through the $30\ \Omega$ resistor in the circuit shown in Figure 1 using nodal analysis method. 7

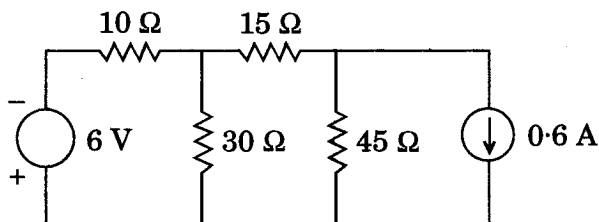


Figure 1

- (b) For the circuit shown in Figure 2, determine the current in the branch AB by using Superposition theorem. 7

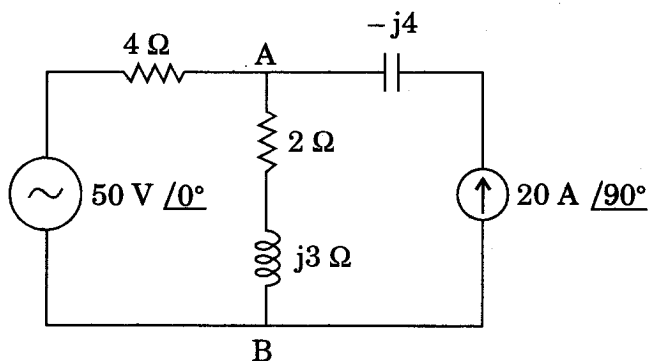


Figure 2

3. (a) For the circuit shown in Figure 3, determine the current through the resistance, inductance and capacitance for $i_s(t) = 10 e^{-2t}$. Take $R = 1 \Omega$, $L = 0.1 \text{ H}$, and $C = 1 \mu\text{F}$. Use Laplace Transform method. 7

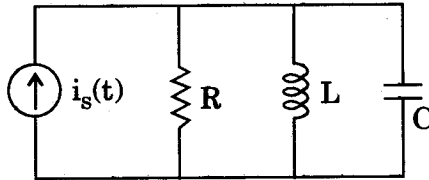


Figure 3

- (b) For the parallel circuit shown in Figure 4, $R = 5 \text{ k}\Omega$, $L = 35 \mu\text{H}$, and $C = 450 \mu\text{F}$. Find the resonance frequency, quality factor, lower and upper cut-off frequencies and bandwidth. 7

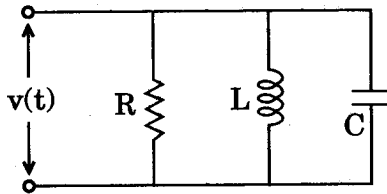


Figure 4

4. (a) For the network shown in Figure 5, determine the transfer functions $G_{21}(s)$ and $Z_{21}(s)$. 7

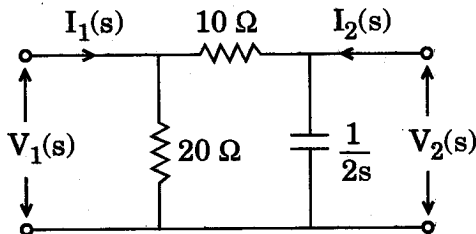


Figure 5

- (b) For the network shown in Figure 6, find the driving point input impedance and plot the pole-zero pattern of the network.

7

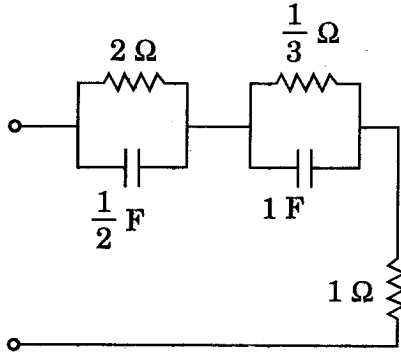


Figure 6

5. (a) Find the Y-parameters for the network shown in Figure 7.

7

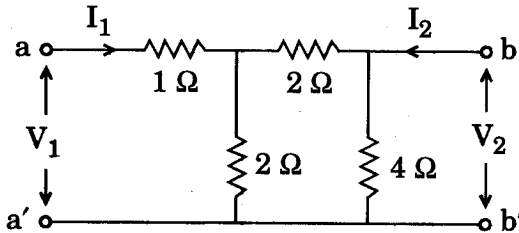


Figure 7

- (b) Obtain the transmission parameters of the circuit shown in Figure 8. Find whether the network is symmetrical or not.

7

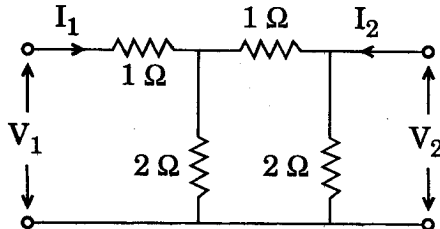


Figure 8

6. (a) Design an m-derived low pass filter having cut-off frequency of 1 kHz, design impedance of 400Ω and resonant frequency of 1100 Hz. 7
- (b) Derive the expressions of characteristic impedance for (i) symmetrical T-section, and (ii) symmetrical Π -section. 7
7. Write short notes on any *four* of the following : $4 \times 3 \frac{1}{2} = 14$
- (a) Source transformation
- (b) Impedance and selectivity in series resonance
- (c) Four-terminal network and its classification
- (d) Solution of RC circuit step response
- (e) Time domain behaviour from pole-zero plot
-