

**DIPLOMA - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING (DECVI) /  
ADVANCED LEVEL CERTIFICATE COURSE IN  
ELECTRONICS AND COMMUNICATION  
ENGINEERING (ACECVI)**

**Term-End Examination**

**June, 2016**

00816

**BIEL-030 : DIGITAL ELECTRONICS**

*Time : 2 hours*

*Maximum Marks : 70*

---

**Note :** Attempt any *five* questions. Question no. 1 is *compulsory*. Use of scientific calculator is allowed.

---

1. Choose the correct answer for the following :  $7 \times 2 = 14$

(a) Convert the following binary number to decimal :

01011

(i) 11

(ii) 35

(iii) 15

(iv) 10

- (b) How many bits are in an ASCII character ?
- (i) 16
  - (ii) 8
  - (iii) 7
  - (iv) 4
- (c) What is the major advantage of ECL logic ?
- (i) Very high speed
  - (ii) Wide range of operating voltage
  - (iii) Very low cost
  - (iv) Very high power
- (d) How is a J-K flip-flop made to toggle ?
- (i)  $J = 0, K = 0$
  - (ii)  $J = 1, K = 0$
  - (iii)  $J = 0, K = 1$
  - (iv)  $J = 1, K = 1$
- (e) How many inputs are required for a 1-of-16 decoder ?
- (i) 2
  - (ii) 4
  - (iii) 8
  - (iv) 16
- (f) The output of an AND gate with three inputs, A, B and C, is HIGH when
- (i)  $A = 1, B = 1, C = 0$
  - (ii)  $A = 0, B = 0, C = 0$
  - (iii)  $A = 1, B = 1, C = 1$
  - (iv)  $A = 1, B = 0, C = 1$

(g) A binary code that progresses such that only one bit changes between two successive codes is

(i) Nine's-complement code

(ii) 8421 code

(iii) Excess-3 code

(iv) Gray code

2. (a) Design a Binary to Gray code converter. 7  
(b) Implement EXOR gate using only NAND gates. 4  
(c) What do you mean by self-complementing code? 3
3. With the help of a diagram, explain the operation of TTL NAND gate with totem pole output. 14
4. Given  $\gamma(A, B, C, D) = \Pi M(0, 1, 3, 5, 6, 7, 10, 14, 15)$ . Draw the K-map and obtain the simplified expression. Realize the minimum expression using basic gates. 14
5. Convert a J-K flip-flop into a D flip-flop and a T flip-flop. 14

**6.** Draw the logic diagram of a 3-bit Serial In Serial Out (SISO) shift register and explain its working. 14

**7.** Write short notes on any **two** of the following :  $2 \times 7 = 14$

- (a) Realization of NMOS inverter
  - (b) Applications of Multiplexer, Demultiplexer and Flip-flops
  - (c) Ring Counter
-