

**DIPLOMA – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)**

00716

Term-End Examination

June, 2016

BIEL-038 : LINEAR INTEGRATED CIRCUITS

Time : 2 hours

Maximum Marks : 70

Note : Attempt any five questions. All questions carry equal marks. Missing data may be suitably assumed. Use of scientific calculator is permitted.

1. Give the block diagram of an op-amp, enlisting the circuit diagram of each block and mentioning the important functions performed by each block. Also draw its ideal voltage transfer curve and pin diagram of IC-741C. 10+4=14

2. Draw the circuit diagram of the following using op-amp and derive an expression for their output voltage : 5+5+4=14

- (a) Difference Amplifier
- (b) Non-inverting Adder
- (c) Non-inverting Amplifier

3. Draw the circuit diagram of an instrumentation amplifier using three op-amp. Also derive an expression for its input impedance, output impedance and voltage gain. $5+3+3+3=14$
4. Draw and explain the operation of the following circuits using an op-amp : $7+7=14$
- (a) Sample and Hold Circuit
 - (b) Schmitt Trigger Circuit
5. Give the circuit diagram of a High pass filter using an op-amp. Derive an expression for its transfer function and hence obtain the expressions for various filter parameters. $5+5+4=14$
6. Explain the operation of the following circuits using IC-555 :
- (a) Monostable Multivibrator
 - (b) Astable Multivibrator
- Support your explanations with the required expressions and output waveforms. $7+7=14$
7. Explain the operation of PLL (IC-565) as
- (a) Frequency Multiplier, (b) FM Demodulator.
- $7+7=14$
8. Write short notes on any *two* of the following : $2 \times 7 = 14$
- (a) Analog Multipliers
 - (b) Comparators
 - (c) Peak-to-Peak Detectors
-