

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00016

Term-End Examination

June, 2016

BIELE-012 : ELECTRONIC SWITCHING CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. All questions carry equal marks. Assume missing data, if any. Use of scientific calculator is permitted.

1. (a) Show how a J-K flip-flop can be converted into a D flip-flop. Explain the change in behaviour by analysing its gate equivalent circuit. 6
- (b) Give the classification of sequential circuits. 4

2. A sequential circuit has two D flip-flops, A and B, two inputs, x and y, and one output, z. The flip-flop input equations and circuits output are as follows :

$$D_A = x'y + xA, D_B = x'B + xA, z = B$$

- (a) Draw the logic diagram of the circuit.
- (b) Tabulate the state table. 10
3. Design a two-input, two-output synchronous sequential circuit, which produces an output $z = 1$ whenever any of the following input sequences occur : 1100, 1010 and 1001. The circuit resets to its initial state after a '1' output has been generated.
- (a) Form the state diagram and state table.
- (b) Draw the logic circuit. 10
4. (a) Determine the conditions under which two equivalent machines are isomorphic. 4
- (b) Prove that, to every q-output, n-state Mealy Machine, there corresponds a q-output Moore Machine which accepts exactly the same sequences and has no more, than $qn+1$ states. 6

5. For the flow table given below, determine all the essential output hazards and essential internal variable hazards.

10

| $x_1 x_2$ | | State, output | | | |
|-----------|-----|---------------|-----|----|----|
| | | 00 | 01 | 11 | 10 |
| ①,1 | 2,0 | 3,1 | ⑤,1 | | |
| 4,0 | ②,0 | 3,1 | 8,1 | | |
| 4,0 | 7,0 | ③,1 | 8,0 | | |
| ④,0 | 6,1 | 9,0 | ⑧,0 | | |
| 4,0 | ⑥,1 | 9,1 | 5,1 | | |
| 1,0 | ⑦,0 | ⑨,1 | 5,1 | | |

6. A memory device has two binary inputs, Y_1 and Y_2 , and three binary outputs y_1 , y_2 and y_3 . When Y_1 is pulse, both y_1 and y_2 are complemented. It is not allowed to pulse Y_1 and Y_2 simultaneously. Use one such device to realize pulse sequential circuit shown in the table.

10

| PS | NS | | Z |
|----|-------|-------|---|
| | x_1 | x_2 | |
| A | D | A | 0 |
| B | C | D | 0 |
| C | A | B | 0 |
| D | B | B | 1 |

7. Prove that if a circuit is designed, so that it is hazard-free in its tie-sets, then it is also hazard-free in its cut-sets. 10
8. Briefly discuss how the static hazards are produced in combinational circuits. How can they be eliminated ? 10
9. Briefly discuss symmetric functions. List all the properties of symmetric functions. 10
10. Write notes on any *two* of the following : 2×5=10
- (a) Contact Network
 - (b) Identification of Symmetric Functions
 - (c) Sequence generator for generating the sequence 01100
-