

**DIPLOMA IN ELECTRICAL ENGINEERING
(DELVI)**

Term-End Examination

00686

June, 2016

BIEE-033 : ELECTRICAL CIRCUIT THEORY

Time : 2 hours

Maximum Marks : 70

Note : Attempt any five questions. Question no. 1 is compulsory. All questions carry equal marks. Use of scientific calculator is allowed. Assume missing data, if any.

1. Write the correct alternative answer. $7 \times 2 = 14$

(a) Internal resistance of an ideal current source is


- (i) infinite
- (ii) zero
- (iii) very low
- (iv) low

- (b) The relationship between voltage and current is same for two opposite directions of current. The network is
- (i) active
 - (ii) bilateral
 - (iii) unilateral
 - (iv) passive
- (c) A terminal where two or more than two branches meet is called
- (i) combination
 - (ii) terminus
 - (iii) anode
 - (iv) node
- (d) The current and power factor of a series resonant circuit is
- (i) maximum, zero
 - (ii) minimum, zero
 - (iii) maximum, unity
 - (iv) minimum, unity
- (e) A $100 \mu\text{F}$ capacitor is connected to a 100 volt d.c. supply. The capacitive reactance of the capacitor will be
- (i) $10^{-6} \Omega$
 - (ii) $1/10^{-6} \Omega$
 - (iii) infinite Ω
 - (iv) 0Ω

- (f) Thevenin's theorem is applicable to
- d.c. circuit only
 - both a.c. and d.c. circuits
 - a.c. circuit only
 - None of the above
- (g) In a star connection, if each resistance is R , then in equivalent delta connection, this value will be
- $3 R$
 - $R/3$
 - R
 - $6 R$

2. (a) Using superposition theorem, determine the current through R_3 .

7

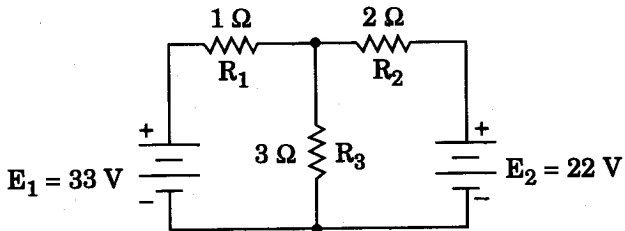

- (b) State and prove the maximum power transfer theorem.


7

3. (a) Derive the condition and find resonant frequency in a series RLC circuit. Also draw the phasor diagram at resonant condition.

7

- (b) An impedance of $(8.66 + j 5) \Omega$ is connected in parallel with another impedance of $(3 - j 4) \Omega$ across a supply of $(80 + j 60)$ volts. Calculate the currents (I_1 and I_2) in each branch.

7

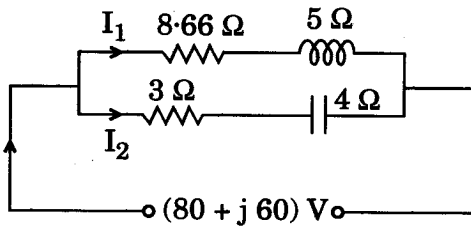

4. (a) Define quality factor, half power frequencies and bandwidth of a resonant circuit. Also draw the current frequency/resonant curve and mark half power frequencies on it.


7

- (b) Draw the power triangle and define active, reactive and apparent power with their units. Also define power factor.

7


5. (a) Find the star equivalent of the given delta connected network.

7

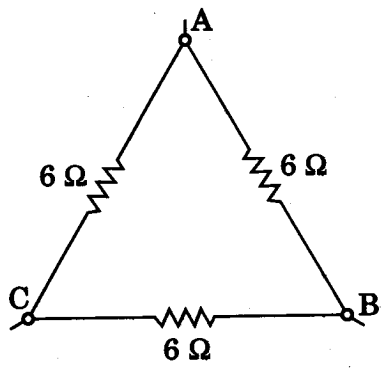

- (b) Find the Norton's equivalent of the Thevenin's equivalent given below and find the value of current flowing through R_L connected across Norton's equivalent network.

7

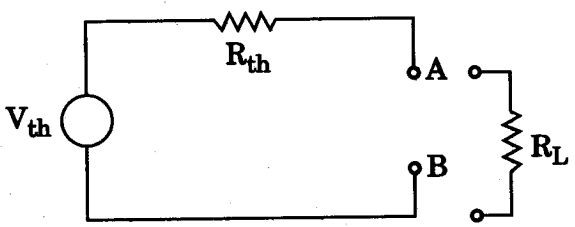


6. (a) Explain Maxwell's loop analysis with the help of a suitable example and neat sketches.

7

- (b) A resistance R is connected in series with a parallel circuit comprising two resistances of $12\ \Omega$ and $8\ \Omega$, respectively. The total power dissipated in the circuit is 70 watts when the applied voltage is 22 volts. Calculate R .

7

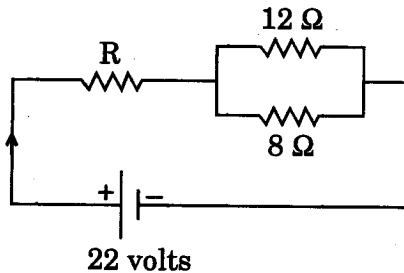

7. Write short notes on any *two* of the following : $2 \times 7 = 14$
- (a) Duality and Dual Networks
 - (b) Source Transformation
 - (c) Concept of Phasor and Complex Impedance
 - (d) Parallel Resonant Circuit
-