

**B.Tech. - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**June, 2015**

**00596**

**BIEL-005 : ANALOG ELECTRONIC CIRCUITS**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any **seven** questions. All questions carry equal marks.*

---

1. (a) Define h-parameters and their limitations. 4  
(b) Determine the current gain, voltage gain, input resistance and output resistance of CE amplifier, if  $R_L = 30 \text{ k}\Omega$ ,  $R_S = 600 \Omega$ ,  $h_{ie} = 2,000 \Omega$ ,  $h_{re} = 1.6 \times 10^{-4}$ ,  $h_{fe} = 49$  and  $h_{oe} = 50 \mu\text{A/V}$ . 6
2. Draw a common base amplifier and its h-parameter equivalent circuit. Derive the expressions for input impedance, voltage gain, current gain and output impedance. 10
3. Draw n-stage CE cascaded amplifier and derive the expressions for voltage gain, current gain, input impedance and output impedance. 10
4. Draw and explain the high frequency transistor model for CE configuration of BJT. Derive the expression for Gain-Bandwidth product. 10

5. Explain push-pull concept and complete operation of Class-B push-pull amplifier, with suitable diagrams. Also mention the distortions in push-pull arrangement. 10
6. (a) Mention the general behaviour of tuned amplifier. Why are these required ? 5
- (b) Differentiate between series and parallel resonance circuits. Derive the formula for circuit impedance at resonance. 5
7. List the negative feedback advantages and explain each with suitable proof. 10
8. (a) Give the classification of oscillators and provide the condition for stability of oscillations. 5
- (b) Comment on tuned-base oscillators and their limitations. 5
9. (a) Define multivibrator and explain the various modes of operation in brief. 5
- (b) Draw and explain the transistorized circuit for astable multivibrator. 5
10. Write notes on any *two* of the following :  $2 \times 5 = 10$
- (a) Darlington Pair
- (b) Wein Bridge Oscillator
- (c) UJT
-