

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00566

Term-End Examination

June, 2015

BIEL-011 : LINEAR INTEGRATED CIRCUITS

Time : 3 hours

Maximum Marks : 70

***Note :** Attempt any **seven** questions. All questions carry equal marks. Missing data may be suitably assumed. Use of scientific calculator is permitted.*

1. Give the circuit diagram of a CASCODE AMPLIFIER (CE-CB configuration). Explain its operation by carrying out its DC Analysis and AC Analysis. 10

2. (a) Give the block diagram representation of a typical op-amp and also enlist the functions performed by each individual stage. 2+3=5

- (b) What are the different arrangements for obtaining positive and negative supply voltages for an op-amp ? 5

3. Explain the frequency response of an internally compensated and non-compensated op-amp. $5+5=10$
4. Define the term slew rate of an op-amp and derive the slew rate equation. An inverting amplifier using 741C has a flat response upto 40 kHz. The gain of the amplifier is 10. What maximum peak-to-peak input signal can be applied without distorting the output? $2+4+4=10$
5. (a) Prove that for an inverting amplifier, the compensation resistor (R_{comp}) placed at the non-inverting terminal to compensate for bias current is given by the expression $R_{\text{comp}} = \frac{R_F R_1}{R_1 R_F}$. 5
- (b) For the circuit shown in Figure 1, determine the magnitude of the output voltage, V_o . 5

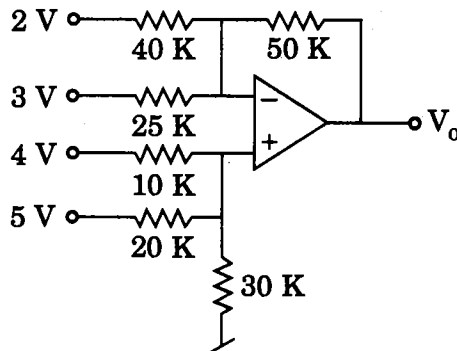


Figure 1

6. (a) Draw the circuit diagram of a voltage to current converter with (i) floating load (ii) grounded load and show that output current is proportional to the input voltage.

i.e. $i_L \propto V_i$

$$3\frac{1}{2} + 3\frac{1}{2} = 7$$

- (b) What is the function of a peak detector circuit? Give its circuit diagram only. 3

7. What are active filters? List the advantages of active filter over passive filter. Prove that the circuit shown in Figure 2 is a first order high-pass filter.

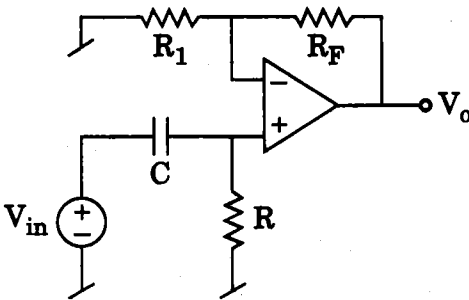


Figure 2

8. For the circuit shown in Figure 3, determine the nature of waveforms at V_{o1} and V_{o2} . Also determine the expression for the frequency of the waveform obtained at V_{o2} . 4+6=10

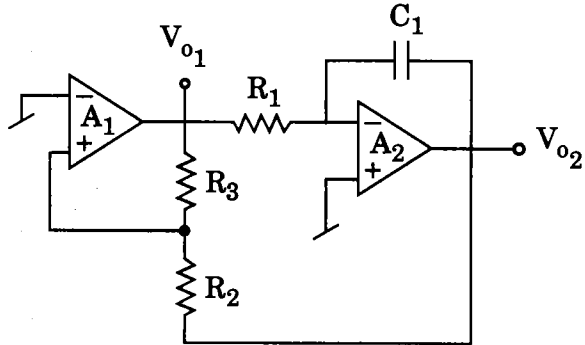


Figure 3

9. Explain the operation of a RC-phase shift oscillator with the help of a neatly labelled circuit diagram and also determine : 5+5=10
- (i) Condition for oscillations
 - (ii) Frequency of oscillations
10. Write the technical notes on any *two* of the following : 2×5=10
- (a) Absolute Value Detectors
 - (b) Clippers and Clampers
 - (c) Small-Signal Full-Wave Rectifiers
 - (d) Zero-Crossing Detectors