

**B.Tech. – VIEP – ELECTRICAL ENGINEERING  
(BTELVI)**

**Term-End Examination**

00866

**June, 2015**


**BIEE-014 : NETWORK THEORY**

*Time : 3 hours*

*Maximum Marks : 70*

**Note :** Attempt any *five* questions. All questions carry equal marks.


1. (a) (i) What is the difference between cut-set and fundamental cut-set matrix ?
- (ii) Explain the procedure of f-cut-set matrix. 7
- (b) (i) State the properties of incidence matrix.
- (ii) Draw the reduced incidence matrix of the directed graph shown in the figure. 7

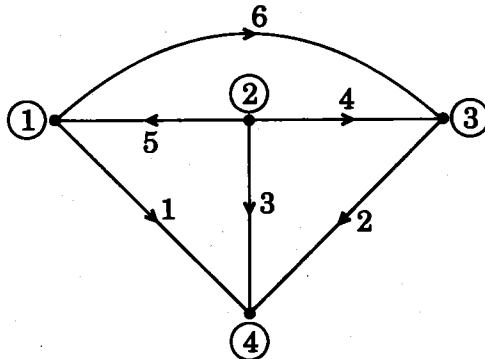

*Figure 1*

2. (a) (i) What is the difference between Thevenin's theorem and Norton's theorem ?
- (ii) Find the Thevenin's equivalent for the network shown below across the terminals AB and hence find the source current.

7

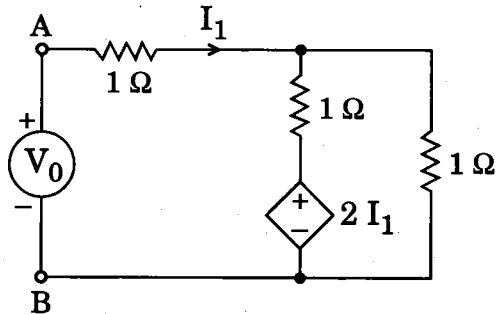

- (b) State and prove Reciprocity theorem.

7

3. (a) The transfer function of a system is given by

$$G(s) = \frac{s^2 + 3}{s(s + 4)(s^2 + 4)}$$

Determine the impulse response of the system.


7

- (b) Define stability. Determine the stability of a system having the following characteristic equation :

7

$$s^6 + s^5 + 5s^4 + 3s^3 + 2s^2 - 4s - 8 = 0.$$

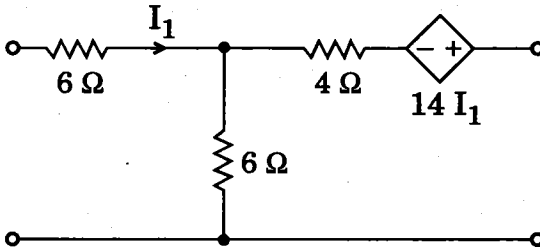4. (a) Find the z-parameters of the network shown in the figure. Hence prove that y-parameters of this network do not exist. 7




- (b) Why are h-parameters known as hybrid parameters ? Discuss the condition of symmetry and reciprocity for h-parameters. 7

5. (a) State the properties of driving point impedance of
- (i) L-C network,
  - (ii) R-C network. 7


- (b) Find the first and second Cauer forms of L-C networks realizing the impedance function

$$Z(s) = \frac{s^4 + 10s^2 + 9}{s^3 + 4s} \quad 7$$

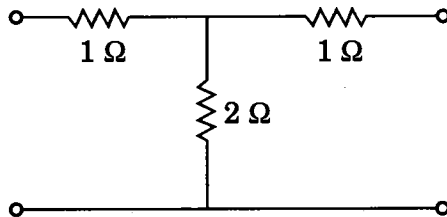6. (a) Find the image parameters of the network shown in the figure. 7



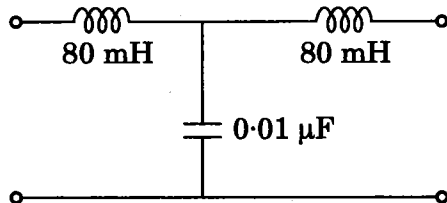- (b) For the given T-section low pass filter, determine the cut-off frequency and normal characteristic impedance  $R_0$ .



Derive the formulae used. 7

7. Write short notes on any *two* of the following :

$2 \times 7 = 14$

- (a) Tellegen Theorem
- (b) Transform Impedance Function
- (c) Ladder and Lattice Network
- (d) Foster-II form of Synthesizing Network
- (e) Advantages and Limitations of Active Filters