

**DECVI / DELVI / DCSVI / ACECVI / ACELVI /
ACSVI**

Term-End Examination

00136

June, 2015

BIEL-027 : APPLIED ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : *Answer five questions in all. All questions carry equal marks. Question number 1 is compulsory.*

1. (a) In Class A operation Q point will be in the mid of _____.
- (b) FET is _____ device.
 - (i) current controlled
 - (ii) voltage controlled
 - (iii) both current and voltage controlled
 - (iv) None of these
- (c) In a parallel tuned amplifier circuit having $R = 10 \Omega$, $L = 20 \text{ mH}$ and $C = 0.05 \mu\text{F}$, the resonance frequency will be
 - (i) 10 kHz
 - (ii) 5 kHz
 - (iii) 17 kHz
 - (iv) 2 kHz

- (d) _____ oscillator has highest frequency stability.
- (e) Transistor operates as an 'ON' switch in _____ region and as an 'OFF' switch in _____ region. 32100
- (f) The function of commutating capacitor is to improve the switching characteristics of the circuit. (True/False)
- (g) Monostable multivibrators are also called monoshot multivibrators. (True/False) 7×2=14
2. (a) Draw and explain the Class A transformer coupled resistive load amplifier. Also find out its efficiency.
- (b) Draw and explain the double tuned amplifier. Also explain its frequency response curve. 2×7=14
3. (a) Draw and explain the Wein bridge oscillator.
- (b) An amplifier with voltage gain of 60 dB uses 1/20 of its output in negative feedback. Calculate the gain with feedback in dB. 2×7=14

4. Draw the output waveform for the following Clipper (Figure 1) and Clamper (Figure 2): $2 \times 7 = 14$

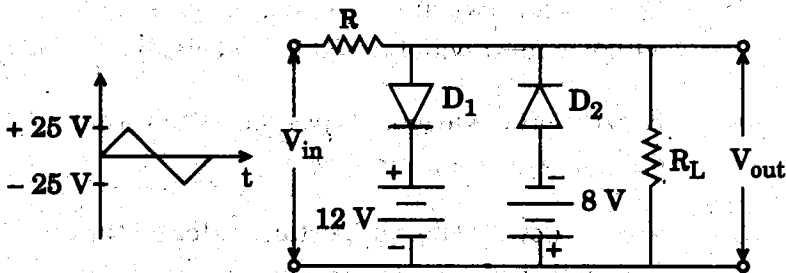


Figure 1

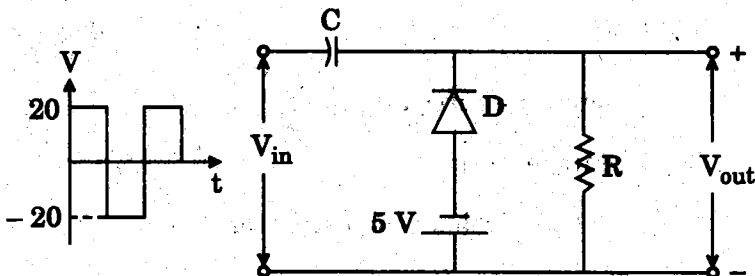


Figure 2

5. (a) Explain the operation of Schmitt trigger with the help of a neat diagram. Also draw the waveform.
- (b) Explain the operation of Astable multivibrator with the help of suitable diagram. $2 \times 7 = 14$

6. (a) Draw and explain the operation of Miller sweep generator.
- (b) Draw and explain the sweep generator which is most widely used in Television. $2 \times 7 = 14$
7. (a) Explain the various types of faults that occur in electronic circuits.
- (b) Write down the important steps that are followed in trouble-shooting of an electronic circuit. $2 \times 7 = 14$
8. Write short notes on any *four* of the following : $4 \times 3 \frac{1}{2} = 14$
- (a) Common source amplifier
- (b) Clamper circuits
- (c) UJT as a relaxation oscillator
- (d) Trouble-shooting of multivibrator
- (e) Classification of power amplifiers
- (f) RC Differentiator circuit
-