

**DIPLOMA - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING (DECVI) /  
ADVANCED LEVEL CERTIFICATE COURSE IN  
ELECTRONICS AND COMMUNICATION  
ENGINEERING (ACECVI)**

**Term-End Examination**

**June, 2015**

00176

**BIEL-030 : DIGITAL ELECTRONICS**

*Time : 2 hours*

*Maximum Marks : 70*

---

*Note : Attempt any five questions. Question no. 1 is compulsory. All questions carry equal marks.*

---

---

1. Attempt all the multiple choice and *True/False* questions.

$7 \times 2 = 14$

- (a) A nibble is equal to 8 bits. [T/F]
- (b) One MB is equal to 1024 KB. [T/F]
- (c) A flip-flop is a sequential circuit. [T/F]
- (d) Ripple counter can be constructed from shift register. [T/F]
- (e) An octal system has
  - (i) 4 digits
  - (ii) 4 bytes
  - (iii) 8 digits
  - (iv) None of the above

- (f) Which is a universal gate ?
- (i) NAND
  - (ii) OR
  - (iii) NOT
  - (iv) None of the above
- (g) How many flip-flops are required for 4-bit register ?
- (i) 2
  - (ii) 3
  - (iii) 4
  - (iv) None of the above

2. Simplify the Boolean function

$$F = \left\{ \overline{\overline{(A+B)} + \overline{(A+B)}} \right\} \text{ using Boolean's law. Also}$$

draw the Logic diagram and make Truth Table. 14

3. (a) (i) Convert the Decimal number 43.125 to Binary.
- (ii) Convert the Decimal number 19.5 to Octal.

$$2 \times 3 \frac{1}{2} = 7$$

- (b) Why is Excess-3 code self-complementary code ? Explain with example. 7

4. (a) Explain and design 3-bit synchronous counter.

- (b) Give the symbol and Truth Table of EX-OR Gate and EX-NOR Gate. Construct an EX-OR gate using NAND gates only.  $2 \times 7 = 14$

5. Simplify the following Boolean function in SOP and POS forms by means of K-map. Also draw the Logic diagram and Truth Table of output function

$$F(A, B, C, D) = \Sigma(0, 2, 8, 9, 10, 11, 14, 15). \quad 14$$

6. What is multiplexer ? What are the applications of multiplexer ? Design a  $16 \times 1$  multiplexer using  $4 \times 1$  multiplexer. 14

7. Draw the diagram of the following flip-flops. Also construct the excitation table :  $2 \times 7 = 14$

- (a) D-flip-flop, T-flip-flop
- (b) Clocked S-R flip-flop with preset and clear, and write the drawbacks of S-R flip-flop.

8. Write short notes on any *four* of the following :  $4 \times 3 \frac{1}{2} = 14$

- (a) A/D and D/A Converter
  - (b) Master Slave Flip-Flop
  - (c) Demultiplexer
  - (d) Moore/Mealy Machine
  - (e) PMOS
-