

**DIPLOMA – VIEP – ELECTRONICS AND  
COMMUNICATION ENGINEERING (DECVI)**

**Term-End Examination**

**June, 2015**

00326

**BIEL-038 : LINEAR INTEGRATED CIRCUITS**

*Time : 2 hours*

*Maximum Marks : 70*

---

*Note : First question is **compulsory** and attempt any **four** from the rest. All questions carry equal marks. Use of scientific calculator is permitted. Missing data, if any, should be assumed.*

---

---

1. (a) A zero-level detector is a  $7 \times 2 = 14$
- (i) Comparator with a sine wave output
  - (ii) Comparator with a trip point referred to zero
  - (iii) Peak detector
  - (iv) Limiter
- (b) A digital-to-analog converter is an application of the
- (i) Scaling adder
  - (ii) Voltage to current converter
  - (iii) Non-inverting amplifier
  - (iv) Adjustable bandwidth circuit

- (c) A Comparator is an example of a(n)
- (i) Active filter
  - (ii) Current source
  - (iii) Linear circuit
  - (iv) Non-Linear circuit
- (d) A two-pole high pass active filter would have a roll-off rate of
- (i) 40 dB/decade
  - (ii) -40 dB/decade
  - (iii) 20 dB/decade
  - (iv) -20 dB/decade
- (e) Duty cycle of an astable multivibrator for  $R_A = 5 \text{ k}\Omega$  and  $R_B = 10 \text{ k}\Omega$  with  $C = 0.05 \text{ }\mu\text{F}$  is
- (i) 0.5
  - (ii) 0.4
  - (iii) 0.6
  - (iv) 0.75
- (f) An instrumentation amplifier should *not* have a CMRR which should be
- (i) Low
  - (ii) High
  - (iii) Zero
  - (iv) Infinite


- (g) A notch filter is a
- (i) Wide BPF
  - (ii) Narrow BPF
  - (iii) Wide band reject filter
  - (iv) Narrow band reject filler

2. (a) Write down the characteristics of an ideal and practical OP-AMP. Draw and explain the ideal voltage transfer curve of an OP-AMP. 7

(b) Explain how the bandwidth of an OP-AMP is changed with feedback. Explain the function of complementary push-pull amplifier in the output stage of an OP-AMP. 7

3. (a) Draw and explain the operation of a practical integrator with necessary derivation. 7

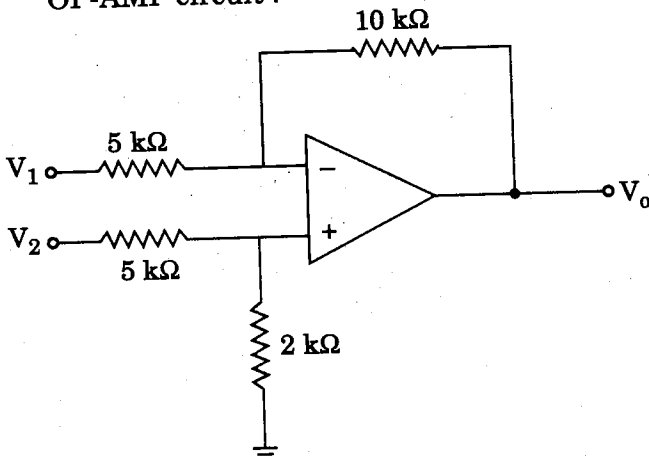(b) Find the output voltage of the following OP-AMP circuit : 7



4. (a) What is the difference between open-loop gain and closed-loop gain of an OP-AMP ? What is the function of unity gain amplifier (voltage follower) ? 7
- (b) Discuss briefly the operation of the sample and hold circuit with required waveforms. 7
5. (a) What is an instrumentation amplifier ? Draw and explain the operation of three OP-AMP based instrumentation amplifiers. 7
- (b) What are the limitations of an active filter ? Plot the response of a typical low pass Butterworth filter and explain the response by identifying the different parameters. 7
6. (a) Design a high pass filter with cut-off frequency 1 kHz and a pass band gain of 2. 7
- (b) Draw and explain the internal block diagram of monostable multivibrator using IC-555 and draw its output waveforms. 7
7. Explain any *two* of the following :  $2 \times 7 = 14$
- (a) IC-565 (PLL) with its applications
- (b) Peak to peak detector
- (c) FM detector

8. (a) Explain how a basic inverting amplifier configuration of an OP-AMP can be used as the following circuits :

7

(i) Sign changer

(ii) Scale changer

(b) Draw and explain the operation of antilogarithmic amplifier (using diodes) with required derivation.

7

