

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(DECVI)**

Term-End Examination

June, 2015

BIELE-006 : ELECTRONIC PRODUCT DESIGN

Time : 2 hours

Maximum Marks : 70

Note : *Question no. 1 is compulsory. Attempt any five questions in all. Each question carries equal marks. Use of scientific calculator is permitted.*

1. (a) Why is thermal consideration necessary for the design of linear regulated power supply ? $7 \times 2 = 14$
- (b) What is P-SPICE ?
- (c) "ROM is a non-volatile memory." Explain.
- (d) Why is cascading of filter required ?
- (e) What are the different types of semiconductor memories ? State their uses.
- (f) What is the function of Voltage Regulator ?
- (g) Write down the various applications of Data Acquisition System.

2. (a) Discuss the limitations of a linear voltage regulator. Explain the indicators for overcurrent and overvoltage in the regulated power supply. 7
- (b) Define power dissipation, thermal equations and efficiency in context of linear regulated power supply. 7
3. (a) Explain the functions of EMI filters and MCB. 7
- (b) Design a 4-bit sequence detector for detecting '1100' in a input string and explain its working. 7
4. (a) Design a combinational circuit using ROM, which generates the cube of a 2-bit number. 7
- (b) Explain the various types of ROM with their applications and internal structure. 7
5. (a) Implement the following function by using PAL : 7
- $$F_1(A, B, C, D) = \sum m (1, 3, 4, 7, 9, 11, 13)$$
- $$F_2(A, B, C, D) = \sum m (0, 5, 6, 10, 12, 13)$$
- $$F_3(A, B, C, D) = \sum m (2, 5, 8, 14, 15)$$
- (b) Design a second order Butterworth High pass active filter for a lower cut-off frequency of 2.5 kHz. 7

6. (a) Explain various realization techniques of Sallen-Key unity gain filters. 7
- (b) Define Butterworth and Chebyshev filters and compare their response. 7
7. (a) Draw and explain the operation of front end analog signal conditioning circuit in microcontroller based Data Acquisition System. 7
- (b) What are the criteria to select suitable Analog to Digital Converter (ADC) for a microcontroller? 7
8. Write short notes on any *two* of the following : $2 \times 7 = 14$
- (a) Moore and Mealy Machine
- (b) KRC Filters Realization Techniques
- (c) 7-Segment LED Display Device Interfacing
-