

B.Tech.

**DECVI / DELVI / DCSVI / ACECVI / ACELVI /
ACCSVI**

00846 **Term-End Examination**

June, 2015

OIEE-001 : BASICS OF ELECTRICAL ENGINEERING


Time : 2 hours

Maximum Marks : 70

Note : *Attempt any five questions. All questions carry equal marks.*

1. (a) A coil is made-up of copper wire. At a temperature of 20°C , the resistance of the coil is $400\ \Omega$. Calculate the resistance of the coil at a temperature of 80°C . The temperature co-efficient of copper is $0.0038\ \Omega/^{\circ}\text{C}$ at 0°C . 7
- (b) State Kirchhoff's current and voltage laws. Explain them with suitable circuit. 7

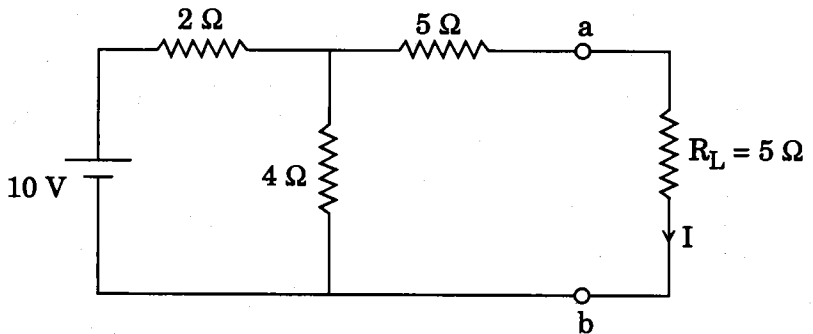2. (a) State and prove Superposition theorem. 7
- (b) Find the current in $R_L = 5 \Omega$ resistor using Thevenin's Theorem. 7



3. (a) Explain the various methods of charging batteries. 7
- (b) Describe the construction of a Lead Acid battery. Write the care and maintenance of a lead acid battery. 7
4. (a) Derive the expression for a force between two parallel current carrying conductors. 7
- (b) Explain the following terms : 7
- (i) MMF
 - (ii) Reluctance
 - (iii) Flux density

5. (a) State and explain Faraday's Law of Electromagnetic Induction. 7
- (b) Define co-efficient of a coupling and calculate it for two coils having self-inductances of 60 mH and 80 mH. The mutual inductance between them is 40 mH. 7
6. (a) Explain the following terms pertaining to ac waves : 7
- (i) Time period
- (ii) Form factor
- (iii) Crest factor
- (b) Define the Average value of a sinusoidal voltage and derive its value. 7
7. (a) A coil of resistance 10Ω and inductance 0.1 H is connected in series with a capacitor of $150 \mu\text{F}$ across 200 V , 50 Hz ac supply. Find the current and power factor of the circuit. 7
- (b) Explain resonance in R-L-C series circuit. 7
8. (a) What are the advantages of 3-phase system over single-phase system ? 7
- (b) Derive the relation between line voltage and phase voltage for 3-phase four-wire system. 7