

**B.Tech. Civil (Construction Management) /
B.Tech. Civil (Water Resources Engineering)**

Term-End Examination

December, 2010


**ET-202(B) : PRINCIPLES OF ELECTRICAL
SCIENCES**

Time : 3 hours


Maximum Marks : 70

Note : Answer any five questions in all. Use of calculator is permissible.

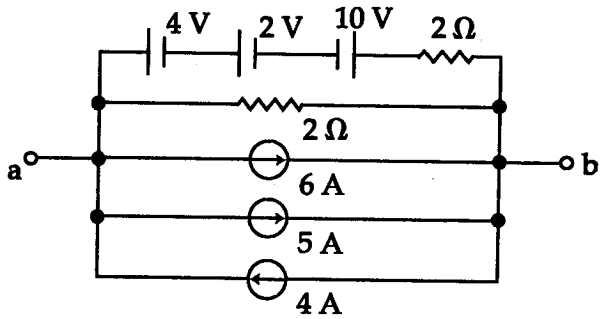1. (a) Define resistance, inductance and capacitance. Give their units, v-i relationship values and specifications for a resistor with uniform geometry an inductor with a toroidal core and a parallel plate capacitor respectively. 6
- (b) State and explain Thevenin's theorem. What is the thevenin equivalent of an ideal d.c. source ? 2
- (c) When are two 2-terminal networks said to be equivalent ? What is the significance of equivalent circuits ? Find simple equivalent for the 2-terminal network shown below : 6



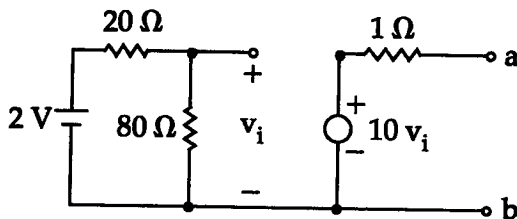2. (a) Explain the following with reference to a 3 phase system : 6
- (i) Meaning of phase sequence,
 - (ii) Function of the neutral wire in the supply system and
 - (iii) Distinction between phase and line voltages.
- (b) What do you understand by the characteristic equation of a system ? What information does it provide regarding the behaviour of the system ? How is it related to the system function ? 4
- (c) Find the Thevenin equivalent at terminals 'a' and 'b' of the active network shown below. 4



3. (a) Give the advantages of three phase system relative to single phase systems. Explain briefly why small electrical loads are designed and built for single phase operation ? 4
- (b) A d.c. machine generates an armature voltage of 220 V on no load at 1000 rpm, the field current being 2A. the armature resistance is 0.5 Ω . Find its speed when it draws a current of 5A as motor from the 220 V supply. (Neglect armature reaction and brush voltage drop) 4
- (c) What is the effect of reversing polarity of the supply voltage on the direction of rotation in the case of the shunt, series and compound d.c. motors ? comment. 6
4. (a) Sketch the typical torque-speed curve of a 3 phase induction motor and identify these on the region of normal operation of the motor. Neglecting stator resistance and stator leakage reactance, show that the maximum torque occurs at a slip of (R_2 / X_2) , where R_2 and X_2 have their usual meanings. 6
- (b) A 3- phase star connected alternator is rated for 5000kVA, 5kV, 50Hz, 150 rpm. It has negligible armature resistance and synchronous reactance of $X_s=1.50$ ohm. Find the induced emf and torque angle when the machine is supplying full load 4

- (c) The following voltages are simultaneously fed to the X-and Y- plates of a CRO 4


$$V_y = 10 \sin 314 t \quad V_x = - \sin 314 t$$

The X and Y deflection sensitivities are 2.5V/cm and 5 V /cm respectively. Sketch the figure that would be observed on the screen of the CRO.

5. (a) A 400 V, 3-phase induction motor runs on no load, drawing a current of 4A from the mains. If the power factor of operation is 0.3 what are the readings of the two wattmeters connected for power measurement ? 4

- (b) Draw the complete circuit of a bipolar junction transistor (BJT) differential amplifier. 4

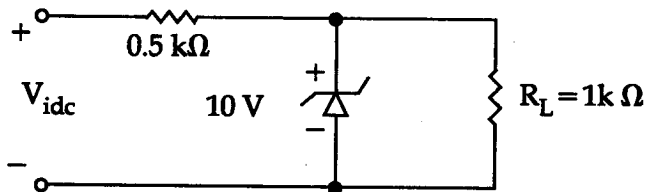- (c) A Zener regulator shown below employs a 10V zener diode with a maximum permissible power dissipation of 50 mW and a knee current of 0.1 mA. Estimate the minimum and maximum permissible limits of the input dc voltage V_{idc} for obtaining regulated voltage. 6



6. (a) Give the circuit diagrams and associated waveforms of a comparators, astable multivibrator and function generator using operational amplifiers. 6
- (b) Draw the circuit of wein bridge oscillator and express the frequency of oscillation in terms of the circuit parameters. 4
- (c) Sketch a 4-bit parallel -m, serial out, shift right register with an initial content of 1001. By means of waveforms and a content table explain its operation through five clock cycles. 4
7. (a) For an 8085 microprocessor. 6
- (i) What does the signal IO/\overline{M} signify and how is it normally used ?
- (ii) What is the function of stack pointer ?
- (b) What is meant by an interrupt in a microprocessor ? List all the interrupts that are available in 8085 microprocessor. 6
- (c) What is analog output voltage of a D-to-A converter corresponding to an input 1101 and $V_r=4V$? 2
-