

## B. Tech. ELECTRONICS AND COMMUNICATION ENGINEERING

### Term-End Examination

December, 2010

### BIEL-003 : DIGITAL ELECTRONICS

*Time : 3 hours*

*Maximum Marks : 70*

*Note : Attempt seven questions in all. Assume any missing data suitably.*

- 
1. (a) Find the 1's and 2's complement of the given number  $(110011.01)_2$  5
  - (b) Convert decimal number 57 in to 5  
(i) Excess - 3 code (ii) Gray code
  2. (a) Minimize the following logic functions and realize using NAND gates 5  
 $f(A,B,C,D) = \sum m(1, 3, 5, 8, 9, 11, 15) + d(2,13)$
  - (b) State and prove De - Morgan's theorem. 5
  3. (a) Design a 4 - digit BCD adder using 7483 binary adder. 5
  - (b) Draw logic diagram of full subtractor and explain its working using Truth Table. 5
  4. (a) Realize the following Boolean expression 5  
using a 8:1 multiplexer.  
 $f(A,B,C) = \overline{A}B C + \overline{A}B\overline{C} + A\overline{B} C + ABC.$

- (b) Draw the logic circuit of Edge triggered JK flip flop and explain its working using truth table. 5
5. Draw the circuit of a 4 bit ripple counter and explain its working. Also draw its timing diagram. 10
6. (a) Draw the circuit diagram of tristate TTL and explain its working. 7
- (b) What are the points to be kept in view while interfacing one logic family to another logic family ? 3
7. Draw a TTL NAND gate circuit with totem pole output and explain its working. Why should it not be used for wired AND connection ? 10
8. (a) Differentiate between static and dynamic RAM. 5
- (b) Use  $16 \times 8$  bit PROM to generate the following function.  $F = \sum m(0, 1, 2, 3, 8, 14)$  5
9. Design an Excess 3 - to - BCD code converter using a 10
- (i) PLA (ii) (PAL) •
10. Write short notes on (*Any two*) : 5x2=10
- (i) Serial - input, Serial - output, shift register.
- (ii) ASCII codes
- (iii) Algorithmic State Machines (ASM)