

**Diploma in Electrical and Mechanical
Engineering**

Term-End Examination

December, 2010

BEE - 042 : ELECTRONICS

Time : 2 hours

Maximum Marks : 70

-
- Note :** (i) *Question no. 1 is compulsory.*
(ii) *Attempt any four questions from the remaining questions numbered 2 to 8.*
(iii) *Use of calculator is permitted.*
-

1. (A) Select the correct answer from the given **Four alternatives.** **7×1=7**
- (i) The region between conduction band and valence band is known as:
- (a) Faraday's region.
 - (b) Crooke's gap.
 - (c) Forbidden gap.
 - (d) Fermi gap.
- (ii) In a reverse bias mode, a diode offers:
- (a) very high capacitance.
 - (b) very high resistance.
 - (c) very low resistance.
 - (d) very low Inductance.

- (iii) The efficiency of a full wave rectifier is :
- (a) 81.2% (b) 40.6%
(c) 20.3% (d) 90.6%
- (iv) In a common emitter configuration of a transistor we get :
- (a) low power gain.
(b) unity power gain.
(c) zero power gain.
(d) high power gain.
- (v) Current gain for a transistor in common base configuration is :
- (a) just less than 1
(b) just greater than 1
(c) much lesser than 1
(d) much greater than 1
- (vi) Decimal equivalent of 0.1011 is :
- (a) 0.5875 (b) 0.6875
(c) 0.6855 (d) 0.5855
- (vii) Full form of I.C. is :
- (a) incorporated circuits.
(b) interfaced circuits.
(c) integrated circuits.
(d) interlinked circuits.


(B) State 'true' or 'false' for the given statements. 7x1=7

- (i) An SCR has an advantage of high switching speed over electromagnetic relay.

- (ii) A series wound DC motor can not exert a high starting torque.
- (iii) Multi channel displaying capacity is possible in dual beam oscilloscope.
- (iv) There is very high electric field in the depletion layer of a p-n junction
- (v) In a common base amplifier the output signal is 180° out of phase with the input signal.
- (vi) When a diode is forward biased its thickness of depletion layer is decreased.
- (vii) Phosphorus is an example of a donor type impurity for doping in semiconductors.

2. (a) Explain the working of Half wave rectifier clearly showing its output & input waveforms. 7
- (b) What is a Zener diode ? Draw its VI Characteristics. 7
3. (a) Let $\alpha = 0.99$ For a BJT. Determine its β . 7
For the same transistor if the emitter current is 1 milliampere , determine the base and collector currents.
- (b) Draw the input and output characteristics of an amplifier in common emitter mode. 7

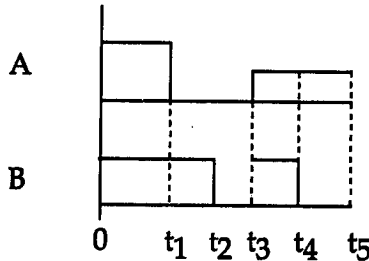4. (a) The following two waveforms are fed to the two inputs of the NAND gate. Draw the output waveform: 7



- (b) How can you make a AND gate using 'OR' gates only ? Explain it. 7
5. (a) Explain the working principle of DC motor as an actuator. 7
- (b) Discuss single phase AC motor as an actuator. 7
6. Discuss SCR with clearly explaining its voltage current characteristics, & voltage safety factor. 14
7. With the help of a diagram explain the working of a monochromatic television transmitter circuit. 14
8. Write short notes on any two of the following: $2 \times 7 = 14$
- (a) Function elements of a generalised measuring system .
- (b) LVDT.
- (c) Turbine flow meter.
- (d) Optical transducer.
- (e) PLC and its applications.