

**DIPLOMA IN VIEP - ECE, EE, CSE,**

**Term-End Examination**

**December, 2010**

**BIEL - 027 © : APPLIED ELECTRONICS**

02184

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any seven questions in all.*

---

1. (a) Distinguish between class - A, class - B, class - C amplifiers. 5  
(b) Draw the circuit diagram of a common source FET amplifier and explain its working in brief. 5
2. (a) Draw circuit diagram of single tuned amplifier and explain its working. 5  
(b) Explain principle of feedback in Amplifiers and list the advantages of negative feedback. 5
3. (a) Explain working principle of RC - phase shift oscillator with the help of neat sketch and write its output frequency expression. 7  
(b) Explain concept of frequency stability in oscillators. 3

4. (a) Explain working principle of RC differentiator with the help of circuit diagram. 5
- (b) For the circuit provided in FIGURE - (1), draw the output voltage waveform. Also name the circuit. 5

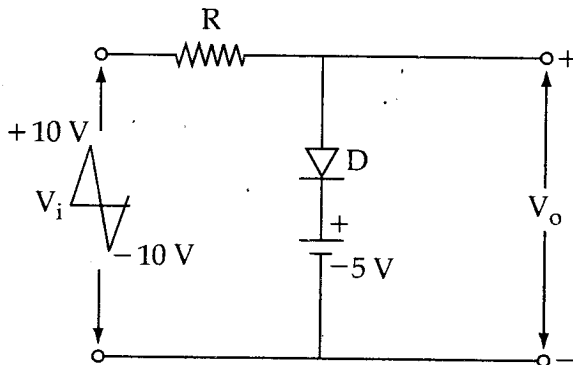


FIGURE - (1)

5. (a) What do you mean by negative clamping ? Explain in detail. 5
- (b) What are different types of multivibrators ? Explain the stable state of multivibrator. 5
6. (a) What are important steps to be taken while trouble shooting and testing of transistorised sweep generator ? 6
- (b) Draw the circuit diagram of a UJT relaxation oscillator and explain it briefly. 4

7. With the help of circuit diagram explain the working of monostable multivibrator circuit. Draw its wave forms. 10
8. (a) What is a time base generator ? Give its classification. 5
- (b) Explain principle of operation of a current time base generator. 5
9. (a) Explain signal analysis active testing method of trouble shooting. 5
- (b) Give applications of time base generator circuit. 5
10. Write short notes on (*any two*) : 5x2=10
- (a) Schmitt trigger
- (b) Crystal Oscillator
- (c) Class AB push pull amplifier.
-