

02584

**BACHELOR OF TECHNOLOGY IN
MECHANICAL ENGINEERING
(COMPUTER INTEGRATED
MANUFACTURING)**

Term-End Examination

June, 2010

**BME-021 : PRINCIPLES OF ELECTRICAL AND
ELECTRONICS SCIENCE**

Time : 3 hours

Maximum Marks : 70

*Note : Answer seven questions. Question no. 1 is compulsory.
Answer any three questions from
Section-A and any three from Section-B. Symbols and
abbreviations carry their usual meaning.*

1. State whether the following assertions are *true* or *false* : 10
- (a) In 8085 Microprocessor, when MOVA, D instruction is executed, the register D still retains the original data.
 - (b) In RS-232, the logic voltages corresponding to logic 0 and 1 are reversed to avoid charge build-up on the lines.
 - (c) If the input to a digital buffer is logic 1, then the output would be logic 0.

- (d) An astable multivibrator can be designed using an OP.AMP. as a comparator.
- (e) A differential amplifier amplifies the difference between two input signals.
- (f) The frequency of a periodic wave is inverse of its time period.
- (g) If C_1 , C_2 , C_3 capacitors are connected in series, then $C_{\text{Equivalent}} = C_1 + C_2 + C_3$.
- (h) In an induction motor the speed of the rotating magnetic field is slightly higher than the rotor speed.
- (i) Reluctance of a magnetic circuit is directly proportional to its length and inversely proportional to its area of cross-section.
- (j) Introduction of an air-gap in a magnetic circuit decreases its reluctance.

SECTION - A

Answer *any three* questions from this section :

2. (a) What is temperature coefficient α ? Give its units. How does the resistance of a metal conductor vary with temperature ? Give a mathematical expression showing change in resistance with change in temperature. **4**
- (b) The tungsten filament of an electric bulb has a resistance of 50 ohms at 0°C . Find its resistance when it is lighted and attains a temperature of 2000°C ; the temperature coefficient at 0°C , α_0 is $0.0045/^{\circ}\text{C}$. **6**
3. (a) State and explain Kirchoff's current law. **4**
- (b) In the circuit of Figure-1, V is 9 volts. **6**
Calculate the voltage V_a at node a using Kirchoff's current law.

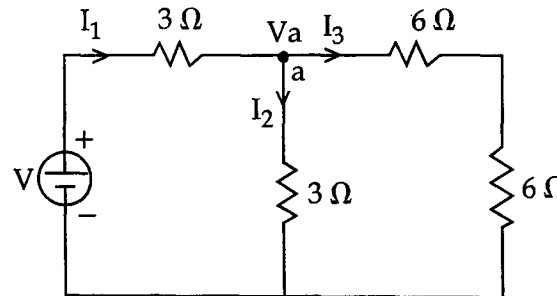


Figure - 1

4. (a) A pure capacitance C is connected in series with a resistance R , and the combination is connected across a voltage source V_s of Frequency f . Write an expression for the current in the circuit. Draw a vector diagram showing voltage drops across R and C , the resultant voltage and current. 5
- (b) In the circuit of Figure-2, V_s is a 169 volt, 50 Hz source with complex impedance of the source as $(5 - j 5)$ ohm. Calculate : 5
- (i) the value of R_L for maximum power transfer to it.
 - (ii) the complex current I_L .
 - (iii) the magnitude $|I_L|$ of current.
 - (iv) P_{\max} the maximum power transferred to load R_L .

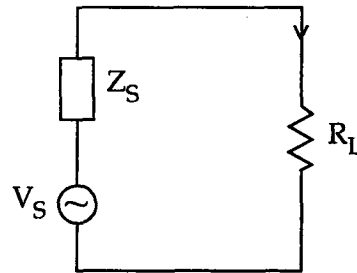


Figure - 2

5. (a) Briefly describe the terms as applied to magnetic circuits : flux density, magnetizing force, relative and absolute permeabilities, giving their units in M. K. S system. Give relation between MMF, S and ϕ in a magnetic circuit and draw analogy to an electric circuit. 4

- (b) A magnetic circuit consists of an iron ring of mean circumference and cross-sectional area respectively of 80 cms and 12 cm^2 . A current of 2 A in the magnetizing coil of 200 turns produces a total flux ϕ of (1.2×10^{-3}) Webers in the iron ring. Calculate :
- (i) flux density B in the iron ring,
 - (ii) the absolute permeability μ ,
 - (iii) relative permeability μ_r
 - (iv) reluctance of the magnetic circuit.
6. (a) Briefly describe : Speed control of induction motors. 2
- (b) A 3-phase, 6-pole induction motor is connected to a 400 volt, 50 Hz supply. Calculate :
- (i) the speed of rotation of the stator magnetic field,
 - (ii) the speed of the rotor when the slip is 5%,
 - (iii) the frequency of the rotor current,
 - (iv) the frequency of the rotor current at stand still.
- (c) What are the different applications of a squirrel cage and wound-rotor induction motors. 2

SECTION - B

Answer *any three* questions from this section :

7. (a) Briefly describe any two . 3
- (i) S–R Flip Flop
 - (ii) J–K Flip Flop
 - (iii) D–Flip Flop
 - (iv) T–Flip Flop
- (b) In which 4 ways can data be shifted in the shift registers. 2
- (c) Give the schematic diagram of a 3-stage ripple counter using T–Flip Flops and show timing signals at the Q_1, Q_2, Q_3 outputs with reference to the clock signal. The Q outputs toggle at negative transition of the clock. 5
8. (a) Briefly describe different busses of an 8085 microprocessor. 2
- (b) What are the different hardware interrupts in the 8085 microprocessor; give their priority. What interrupt is non-maskable. 3
- (c) What operations do the following 8085 microprocessor instructions perform ? (write about any five). 5
- (i) MOV C, B
 - (ii) ADI F2H
 - (iii) ORI 66H
 - (iv) JMP 2050H
 - (v) ANI 80H
 - (vi) CMA
 - (vii) XRA C
 - (viii) HLT
 - (ix) NOP

9. (a) What do α and β , in bipolar junction transistors, represent; derive an equation giving their relationship. 3
- (b) Give the circuit schematic and gain equation of an I. C. operational amplifier in inverting configuration. 3
- (c) Give the value of the feed-back resistance R_2 to obtain a gain of 20 dB, if $R_1 = 1 \text{ k}\Omega$ is connected between the signal input and the OP.AMP.'s inverting input. 4
10. Write short notes on *any two* of the following : 10
- (a) TRIAC (b) MOSFET
- (c) IGBT (d) Zener diode
11. (a) Give schematic diagram of an astable multivibrator using the 555 timer I. C. Show how external resistances R_A (connected between supply and pin 7), R_B (connected between pin 6 and pin 7) and external capacitor C (connected between pin 6 and ground) are used to obtain T_H (High) and T_L (Low) time periods for the generation of the output wave form. 4
- (b) How would you generate a near square wave using the above timer I.C ? 2
- (c) Calculate the value of the capacitor C , shown as above in the 555 timer, to generate a square wave of 5 kHz, if $R_A = R_B = 50\Omega$. 4