

**B. Tech. ELECTRONICS AND
COMMUNICATION ENGINEERING**

Term-End Examination

June, 2011

BIEL-003 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : Attempt seven questions in all. Assume any missing data suitably.

-
1. (a) State and prove De Morgan's Theorems. 5
(b) Convert the gray code number 110011 to binary. 5

 2. (a) Minimize the following function using K-map and realize using minimum number of gates. 5
 $F(A, B, C, D) = \sum m(0, 1, 2, 3, 11, 12, 14, 15)$
(b) Design a half adder circuit using gates. 5

 3. (a) Realize the following function using 8 : 1 multiplexer. 5
 $F(A, B, C, D) = \sum m(0, 1, 2, 3, 11, 12, 14, 15)$
(b) Convert the given boolean function into canonical SOP form 5
 $F(A, B, C, D) = \bar{A}BC + A\bar{D} + ACD$

4. (a) Draw logic diagram of 4 bit adder/subtractor and explain its working. 5
 (b) What is the race - around condition in JK flip flop ? How it can be overcome ? 5
5. Design a 3 - bit Synchronous up down counter using J - K flip - flops. 10
6. (a) Explain working of MOSFET as switch. 5
 (b) Draw circuit diagram of CMOS - NOR gate and explain its working. 5
7. (a) Explain various specifications of digital ICs. 4
 (b) What is wired AND connection of digital ICs ? What are its advantages ? Draw a circuit of TTL NAND gate with wired AND connection. 6
8. (a) Draw a ROM array and explain its working principle. 5
 (b) Explain Concept of PAL. 5
9. Design a BCD to seven segment decoder using
 (a) PROM (b) PLA 5x2=10
10. Write short notes on (*any two*) 5x2=10
 (a) ASCII code
 (b) Digital Comparator
 (c) Pseudo Random Binary Sequencing (PRBS) generator.