

**B.Tech. Civil (Construction Management) /
B.Tech. Civil (Water Resources Engineering)**

Term-End Examination

June, 2011

**ET-202(B) : PRINCIPLES OF ELECTRICAL
SCIENCES**

Time : 3 hours

Maximum Marks : 70

Note : Answer any five questions. Symbols and abbreviations have their usual meaning. Use of calculator is permitted.

1. (a) Explain the principle of superposition theorem. 6
- (b) Find the current drawn from the battery source for the circuit shown in Fig. 1. 8

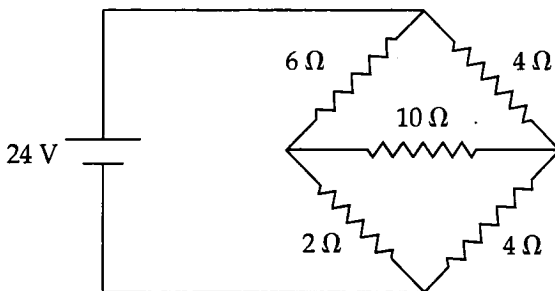


Figure - 1

2. (a) Express the following phases in 3+3
(i) rectangular and (ii) polar coordinate
 $V(t) = 200 \sin(\omega t + 60^\circ)$

- (b) Draw the power triangle comprising Real Power P , Reactive Power Q and Apparent Power S . 3
- (c) A 440 V, 50 Hz, 4 pole, three phase induction motor is rotating at a speed of 1440 rpm. Find the percentage slip. 5
3. (a) Explain the operation and characteristics of dc shunt motor. Give its applications. 6
- (b) Explain the principle of operation of single phase transformer. Mention the salient differences between (i) Power transformer, (ii) Distribution transformer in their construction and operation. 6
- (c) What is instrument transformer ? State its special features. 2
4. (a) Name the instruments required to measure. 4
- (i) Alternating current (ac)
 - (ii) Direct current, (dc)
 - (iii) ac voltage
 - (iv) dc voltage
 - (v) dc power,
 - (vi) ac power,
 - (vii) dc energy
 - (viii) ac energy

- (b) State and describe briefly ten (10) components used in a typical industrial electrical installations. 5
- (c) Draw the schematic block of a typical large unit for an industry. Explain its parts in brief. 5
5. (a) Draw and explain a full wave diode based rectifier circuit, with waveforms. 5
- (b) Explain the operation of transistor as an amplifier. 5
- (c) An opamp has 60 dB gain. The output voltage of the differential amplifier is 10 volt. Determine the input voltage. 4
6. (a) Draw a Half-Adder, state its truth table and explain the operation. 5
- (b) Find the decimal equivalent of $(101010)_2$. 3
- (c) What is Stack Pointer, Program Counter, Interrupt and Register as applied to microprocessor. 6
7. (a) Write short notes on *any two* : 6+6
- (i) Rectifier instrument
- (ii) Synchronisation
- (iii) Speed control of dc series motor
- (iv) Cathode Ray Oscillator (CRO)
- (b) The reading of two watt meters connected to measure three phase power consumption gave the reading as
 $W_1 = -350$ Watt $W_2 = 1200$ Watt
 Calculate the power factor of the load. 2