

**DIPLOMA IN ELECTRONICS AND
COMMUNICATION ENGINEERING
(DECVI/DELVI/DCSVI)**

Term-End Examination

June, 2011

BIEL-027 : APPLIED ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : Question No. 1 is *compulsory*.

Attempt any five Questions.

Each Question carry equal marks.

-
1. This part consists of fill in the blanks, objective type questions and True/False.
- (a) An amplifier with negative feedback has **2**
_____ bandwidth than (as) the
amplifier without feedback.
- (b) Full form of MOSFET is called _____ **2**
- (c) With feedback β , the overall gain of the **2**
circuit is reduced by a factor _____
where A is the gain without the feedback.
(i) β (ii) $A\beta$
(iii) A (iv) $1+\beta A$
- (d) For a phase-shift oscillator, the gain of the **2**
amplifier stage must be greater than

(i) 19 (ii) 29 (iii) 30 (iv) 1

- (e) Which of the following oscillator is tuned oscillator ? 2
- (i) Colpitts Oscillator
 - (ii) Phase-shift Oscillator
 - (iii) Wein Bridge Oscillator
 - (iv) Pierce Oscillator

State True or False

- (f) In series resonant circuit, at resonant frequency, the circuit impedance is minimum. 2
- (g) Field - Effect transistor is a bipolar device that is the current in the device is carried by both electrons and holes. 2
2. (a) How are the power amplifiers classified ? 7
 Explain each type. Draw the circuit diagram of a class B push-pull amplifier with its working.
- (b) What is the significant difference between the construction of an enhancement type MOSFET and depletion type MOSFET ? 7
 Show that the transconductance g_m of JFET is related to drain current I_{DS} by

$$g_m = \frac{2}{V_p} \sqrt{I_{DSS} I_{DS}}$$

3. (a) What is a tuned amplifier ? What are the objectives or merits served by tuned amplifier ? Compare the frequency response of single tuned and double tuned amplifiers. 7
- (b) Explain the meaning of resonance curve. Plot a resonance curve for a parallel tuned circuit and also derive an expression of resonance frequency of a parallel tuned circuit. A parallel resonant circuit has a bandwidth of 15 KHz and Q factor of 120. What is the resonant frequency of the circuit ? 7
4. (a) Discuss the advantages of negative feedback on voltage gain, stability, distortion, bandwidth, output and input impedance of an amplifier, 7
- (b) Draw an emitter follower and explain its working. Why it is called emitter follower ? Which type of feedback is being realized in emitter follower ? 7
5. (a) What is Barkhausen criterion for oscillation ? Describe the principle of operation of a Wein Bridge Oscillator and give the condition for sustained oscillation. 7

- (b) Explain why : 7
- (i) Three RC sections are used in R-C phase shift oscillator with diagram.
 - (ii) Negative feedback is employed in Wein - Bridge oscillator in addition to usual positive feedback.
 - (iii) A negative feedback is always employed in high gain amplifiers.
6. (a) (i) What is a Schmitt Trigger ? Why is it called a regenerative comparator ? Define V_{UT} , V_{LT} and hysteresis in Schmitt Trigger 7
- (ii) Draw the circuit of astable multivibrator. Explain its working briefly.
- (b) Write short notes on : 7
- (i) Clampers
 - (ii) Miller sweep generator
7. (a) What is a differentiator ? How is it different from integrator ? List out the applications of integrator. 7
- (b) What is negative resistance generator ? List out the points for the troubleshooting of multivibrators, transistorised sweep generator, clipping and clamping circuits. 7