

**DIPLOMA IN ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)**

Term-End Examination

00832

June, 2011

BIEL-028 : CIRCUITS AND NETWORKS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any five questions. Each questions carry equal marks.

1. Attempt any two parts.

14

- (a) Determine the voltage across the 10Ω resistor using Nodal analysis in fig 1.

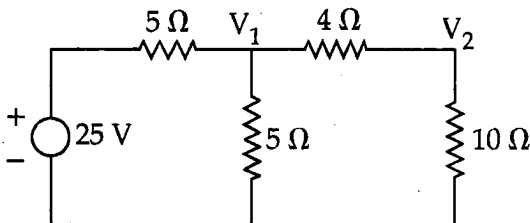


Fig. 1

- (b) Discuss the source transformation for dependent sources.

- (c) Determine the current in Branch BD where galvanometer is connected in fig. 2.

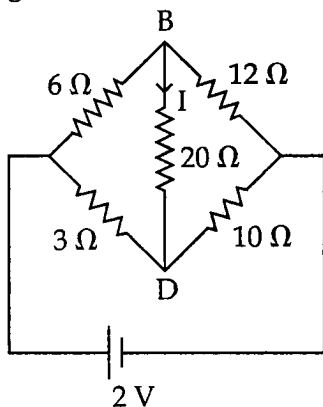


Fig. 2

2. Attempt *any two* parts. 14

- (a) Discuss the Natural Response of RC Network and also find the characteristic equation of RC Network.
- (b) Determine the current through the Inductor L for $t \geq 0$ as a parallel RL circuit. The switch is been in position 1 for a long time and then moved to position 2 at $t=0$ circuit shown in fig 3.

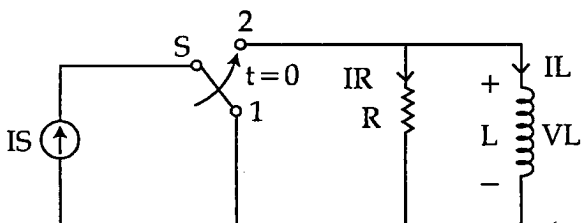


Fig. 3

- (c) Explain the series resonance in the circuit also discuss the figure of merit.

3. Attempt *any two* parts.

14

- (a) Draw the Thevenin's equivalent of the circuit given in and find the load current in $2\ \Omega$ resistor. fig 4

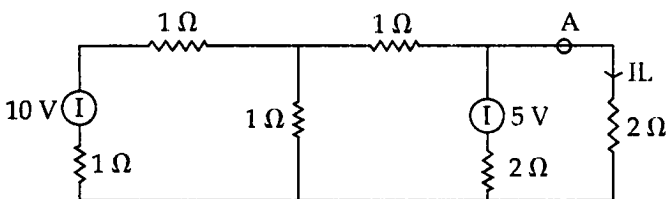


Fig. 4

- (b) Discuss the maximum power transfer theorem and prove maximum power will be $P = E^2/4R$.
- (c) Determine current through $5\ \Omega$ Resistor using Norton theorem in fig. 5.

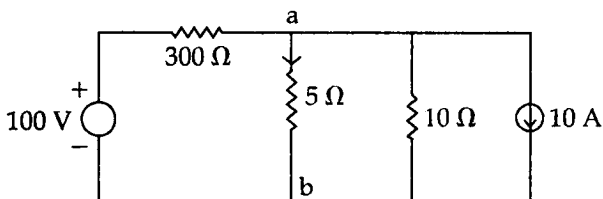


Fig. 5

4. Attempt *any two* parts.

14

(a) Discuss the significance of pole and zero in Network functions.

(b) If $F(s) = \frac{S(S+1)}{(S+4)(S^2+4S+Q)}$

Find $f(t)$ using the pole-zero diagram of the functions.

(c) Discuss the Necessary condition for transfer function also discuss the pole position on the system stability.

5. Attempt *any two* parts.

14

(a) Find the Z parameters for the π Network in Fig 6.

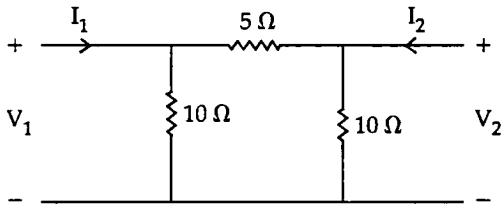


Fig. 6

(b) Determine the h parameters for the Network in fig 7.

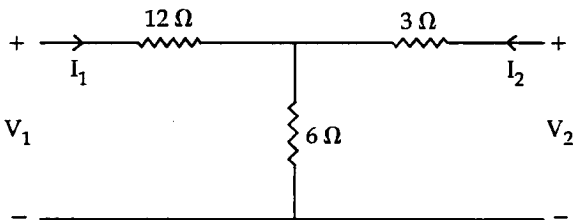


Fig. 7

- (c) Determine ABCD parameters for the Network in fig 8.

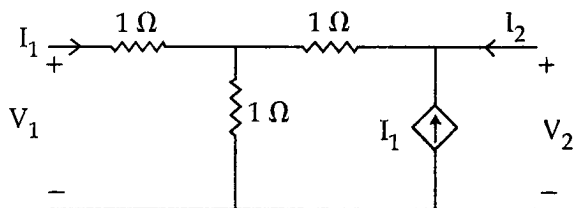


Fig. 8

6. Attempt *any two* parts : 14
- (a) Discuss series series inter connection of two port Networks.
 - (b) Explain impedance transformation in resonance circuits.
 - (c) Discuss super position theorem with example. How it is helpful in Network analysis.
7. Attempt *any two* for writing short notes. 14
- (a) T- Type Attenuator
 - (b) Constant K - Type Low Pass Filter.
 - (c) Hybrid Parameters.
 - (d) Series Resonance Circuit.