

**DIPLOMA IN ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)**

00024

Term-End Examination**June, 2011****BIEL-030 : Digital Electronics***Time : 2 hours**Maximum Marks : 70*

Note : *Attempt any five questions. Each carry equal marks.
Question no one is compulsory (objectives). Give answer
precisely and accurate.*

1. Attempt all objectives questions. **7x2=14**
- (a) 1^s complement of the 101011 is
- (i) 010100 (ii) 000000
(iii) 111111 (iv) 100000
- (b) The expression \overline{ABC} can be simplified
- (i) $\overline{A} B \overline{C}$ (ii) $AB + BC + CA$
(iii) $AB + \overline{C}$ (iv) $\overline{A} + \overline{B} + \overline{C}$
- (c) The Universal gates are
- (i) NAND and NOR
(ii) AND and OR
(iii) OR and X-OR
(iv) None

- (d) 3x8 Decoder have
- (i) 3 I/p^s and 8 O/p^s
 - (ii) 8 I/p^s and 3 O/p^s
 - (iii) 8 I/p^s and 8 O/p^s
 - (iv) none
- (e) The following is not a sequential circuit.
- (i) J-K flip-flop
 - (ii) Counter circuit
 - (iii) Full adder
 - (iv) Shift Register
- (f) MUX have
- (i) many I/p^s and one O/p
 - (ii) one I/p^s and many O/p^s
 - (iii) one I/p^s and one O/p
 - (iv) None.
- (g) Combinational circuits are designed with.
- (i) feedback
 - (ii) without feedback
 - (iii) either (i) or (ii),
 - (iv) None.

2. (a) Converts the following base. **2x7=14**

- (i) $(1010.11)_2 = (P.)_8 = (P.)_{16} = (P.)_{10}$
- (ii) $(3AE5)_{16} = (P.)_8 = (P.)_{10} = (P.)_2$
- (iii) Add $(3269)_{12} + (2368)_{12}$ without changing base

(b) Realize the following function using basic gates.

- (i) $Y = ABC\bar{C} + \bar{A}BC + ABC$
- (ii) $Y = ABCD + \bar{A}BC\bar{D} + ABC\bar{D}$

3. (a) Converts the following into canonical form. **2x7=14**
 (i) $AB + BC + CA$
 (ii) $(A + B). (B + C). (C + A)$
 (b) Minimize the following using K-MAP.
 (i) $f(w,x,y,z) = \sum m(0,1,2,4,5,6,8,9,12,13,14)$
 (ii) $F(A,B,C,D) = \sum \pi(2,3,4,5,6,7,11,14,15)$
4. (a) Design a gray to binary converter ckt of 3 bit (variable). **2x7=14**
 (b) Write the steps for combination ckt Design and design a full adder ckt with basic gates.
5. (a) Give difference between combinational ckt and sequential ckt and Design a S-R flip-flop Using NAND gates. **2x7=14**
 (b) Design a Asynchronous MOD 8 counter ckt.
6. (a) Design a 8×1 Multiplexer circuit and give the application of MUX. **2x7=14**
 (b) Design a 4 bit shift Register ckt.
7. Write the short notes on *any two*. **14**
 (a) Propagation delay and Fan In and Fan out
 (b) C MOS Inverter ckt.
 (c) TTL logic family.
 (d) EPROM and EEPROM.
-