

**DIPLOMA - VIEP - ELECTRICAL  
ENGINEERING**

**Term-End Examination**

**June, 2011**

**BIEE-027 : ELECTRICAL MACHINES - I**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Five questions are to be answered. Each question carries  
14 marks. Use of scientific calculator is permitted.*

---

1. Explain the process of commutation in a dc machine and discuss the methods to improve it. 14
  
2. Explain the voltage build up process in a dc shunt generator. Describe with relevant diagrams the different methods of excitation of dc machines. 14
  
3. (a) Draw the external characteristics of dc separately and shunt excited generator. Which one has more drooping characteristics and why? 7
  
- (b) A 400 V dc shunt motor takes a current of 5.6 A on no load and 68.3 A on full load. Armature reaction weakens the field by 3% calculate the ratio of full load speed to no load speed. Given  $R_a = 0.18 \Omega$ , brush voltage = 2V and  $R_f = 200 \Omega$  7

4. A dc motor takes an armature current of 50 A at its rated voltage of 240 V. Its armature resistance is  $0.2\ \Omega$ . If an external resistance of  $1\ \Omega$  is inserted in series with the armature and the field flux remains unchanged. Calculate 14
- (a) % decrease or increase in speed for the same load torque.
  - (b) % decrease or increase in speed for half of the load torque.
5. Explain the regenerative method of determining the efficiency of a dc machine. List the merits and demerits of this method. 14
6. Draw and explain the equivalent circuit of a single phase transformer. 14
7. Explain the open circuit test and short circuit test of a transformer. 14
8. A 100 kVA, 3 phase, 50 Hz, 3300/400 V. Transformer is delta connected on the hv side and star connected on the lv side. The resistance of the hv winding is  $3.5\ \Omega$  per phase and that of lv winding is  $0.02\ \Omega$  per phase. Calculate the iron losses of the transformer at normal voltage and frequency if its full load efficiency be 95.8% at 0.8 pf (lag). 14
9. Briefly explain the polyphase connections 3 phase to 2 phase, 3 phase to 6 phase and 3 phase to 12 phase. 14
10. Write a short note on *any two* of the following. 7, 7
- (a) Auto transformer
  - (b) Connections in a 3 phase transformer
  - (c) Lap and wave winding